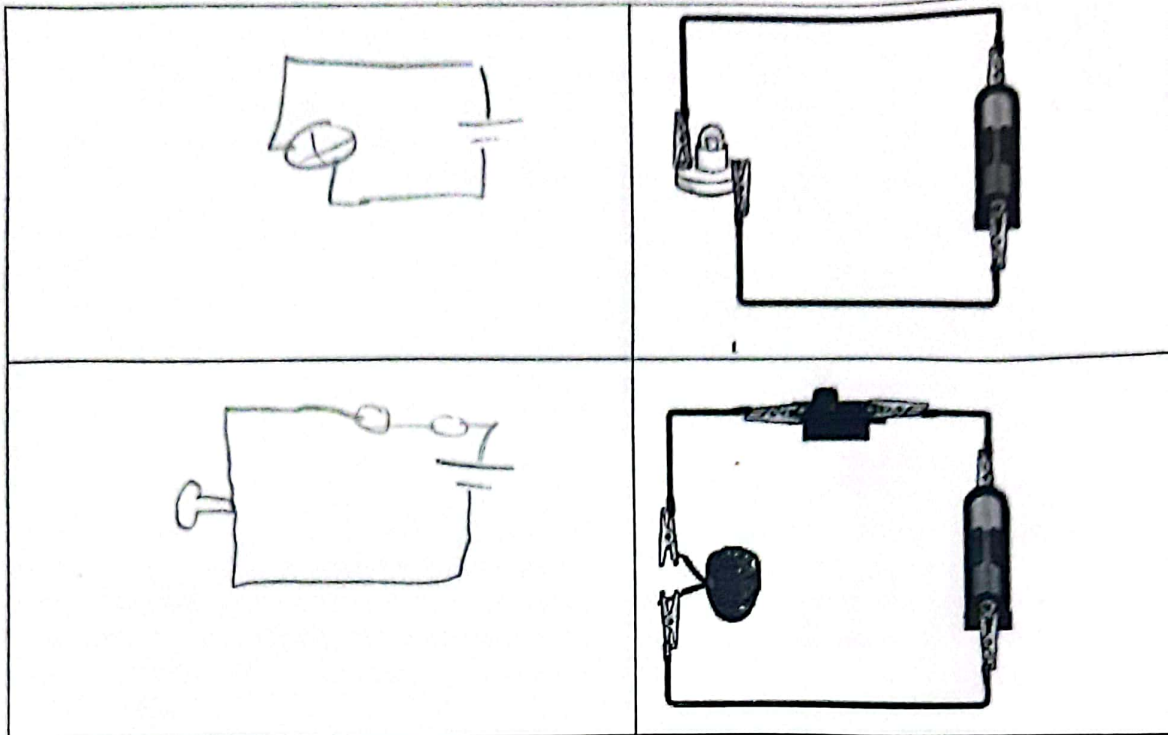
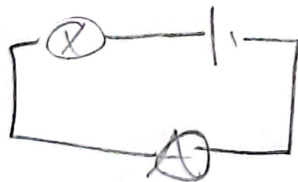


Draw the following circuits using the scientific circuit symbol:



Draw the following circuits using the scientific circuit symbols:

A) Circuits should contain: a bulb, a cell, an ammeter



B) Circuit should contain: a three celled battery, two motors each working separately with a way to turn each one on/off in addition to ammeters and voltmeters

