

# Science Worksheet #1 / Term 2


## Investigating batteries/ Describing electric circuits

Name: Answer Key


Grade 8 ( )

Date: /02/2023

1 – Label the following diagram.

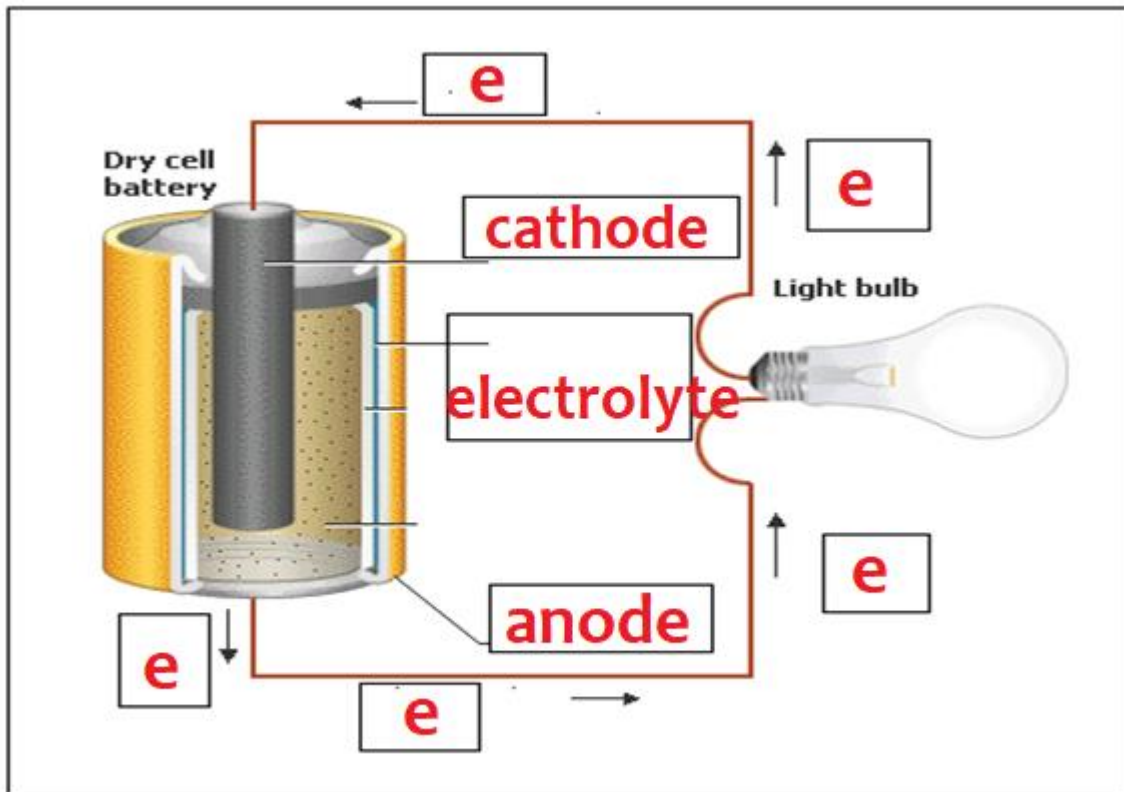

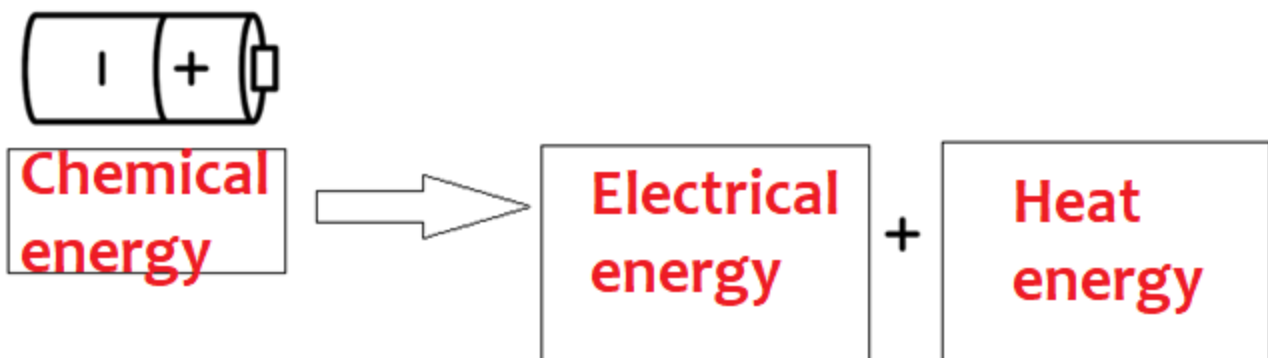2- Complete the following energy transfer diagram showing changes taking place in a battery.



**3- Study the following fruit battery, and then answer the following questions.**



a- Draw the flow of the electric current in this battery.

b- The zinc nail represents the: **anode** **cathode**

c- Name the device you would use to measure the voltage across this circuit.

**Voltmeter**

d- Can you think of other ways of increasing the voltage of a fruit battery?

**Increase the juice so use a fruit with more juice.**


**Decrease the distance between the metals**

**Change the metals**


e- Explain the following statement: 'A battery will not work with dried fruit.'

**The liquid will enable the electrons to move and take part in the chemical reactions.**

4- Name the following circuit symbols.

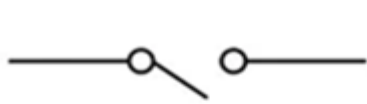

switch (open)

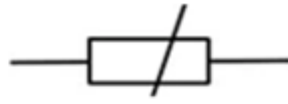


variable  
resistor



lamp



switch (closed)

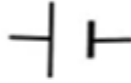


cell



ammeter



resistor

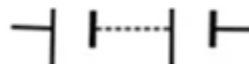

battery



voltmeter



5- Which of the following are likely to be conductors and which will be insulators?

copper iron brass plastic carbon (graphite) glass


**Conductors: copper/ iron/ brass/ carbon**

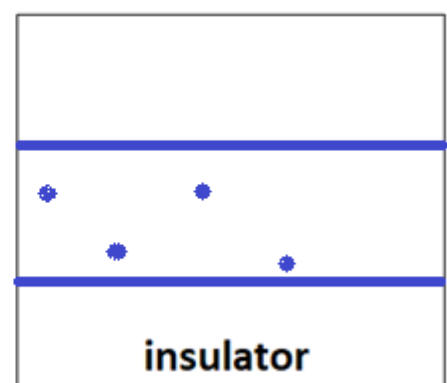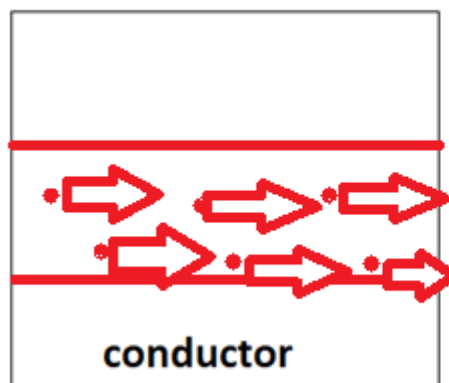**Insulators: plastic/ glass**

- Draw a model to represent an electrical insulator and an electrical conductor, to explain the meaning of these two terms.



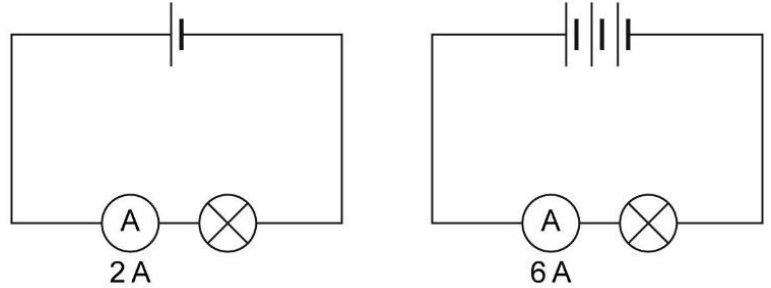- Explain the differences in current in the two circuits shown below.



**The second circuit has more cells which means that increasing cells produces larger current.**

---