



The National  
Orthodox School  
Shmaisani

## The National Orthodox School /Shmaisani

**Subject: Physics**

**Title: Ohm's Law**

**Name:**

**Grade-Section: 8 CS \_\_\_\_\_**

**Date:**

**Mark: \_\_\_\_/5**

Solve the following questions showing your work:

- 1) What is the resistance of a component if the current going through it is 36A and the voltage across it is 12V?
- 2) What is the voltage across a component with a resistance of  $130 \Omega$  that has a current of 2.5A going through it?
- 3) What is the current through a component if the component has a resistance of  $4.5 \Omega$  and the voltage across the resistor is 60V?
- 4) If the current through a  $10\Omega$  component is 16A, what is the voltage across the component?
- 5) What voltage is necessary to produce a current of 200 amperes through a component of  $10 \Omega$ ?

